

# Basic Electronics

## Assignment 3 – Virtual lab

### Experiments:

1. RC Differentiator and Integrator
2. Studies on BJT CE Amplifier

Reported by :

- 1.Chandushree H S
- 2.Charan N N
- 3.Charanya A
- 4.Chetan T J

